Combination circuits

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Reduce a circuit by identifying genuine series and parallel groups.

SUCCESS CRITERIA - I can...

1. Identify nodes before grouping resistors.
2. Reduce one group at a time.
3. Check current and voltage conservation in the original circuit.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

01 Warm-up: bring back an earlier idea

A **3 Ω** resistor carries **5 A**. **Find the potential difference across** it.

Marzano check - circle: ① ② ③

02 Worked example: explain the prediction

Reference: $R_{series} = R_1 + R_2$; $\mathbf{1}/R_{parallel} = \mathbf{1}/R_1 + \mathbf{1}/R_2$; $V = IR$. Reduce one known group at a time. **Check nodes before calling components** series or parallel.

Worked reasoning: A **2 ohm** resistor is in series with two **4 ohm** resistors in parallel. The parallel pair equals **2 ohms**; total **4 ohms**. A **12 V** supply gives **3 A** total.

Your turn: Draw the network and **label the two series sections** before splitting the branch current.



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

03 Read and explain the diagram or equation

A **2 Ω** resistor is in series with two parallel **6 Ω** resistors. **Draw the arrangement** and circle the parallel group.



Circuit symbols: long/short lines = battery; rectangles = resistors.

Marzano check - circle: ① ② ③

04 Apply the physics

A **10 V** battery powers the network in question **3**: a **2 Ω** resistor in series with two parallel **6 Ω** resistors. You may use the supplied parallel equivalent, **3 Ω**. **Label each section**, find total resistance and **calculate source current**.



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

Combination circuits

antocciphysics

Continue down each column.

05 Explain your reasoning

A student adds all three resistor values because they are drawn side by side. What should find the grouping instead?

Marzano check - circle: ① ② ③

06 Review: connect an earlier idea

A radar echo’s complete outward-and-return path is **6000 m**. **Find the target range** and **explain the division**. **Label the outgoing** and returning paths.



Marzano check - circle: ① ② ③

07 Exit check

If **2 A** reaches two equal parallel branches, find each branch current. **Label the circuit** and **show the current path or** paths.




Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

08 STRETCH: test the prediction

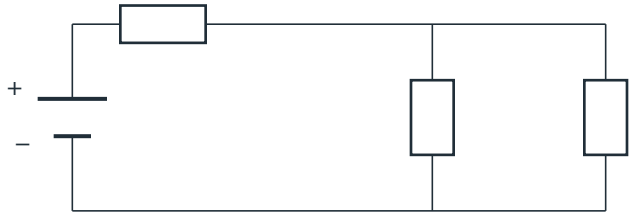Return to the worked example in problem **2**. Replace the parallel pair by two **8 ohm** resistors.
1. **Find the new equivalent resistance** and total current on **12 V**.
2. **Label the circuit** and **show the current path or** paths.



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③