Simulate a circuit and practice soldering

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Test a circuit representation before making permanent connections.

SUCCESS CRITERIA - I can...

1. Build a complete battery-switch-motor circuit in the simulation.
2. Explain an open versus closed path.
3. Document a supervised solder-practice check.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

01 Warm-up: bring back an earlier idea

A car receives **50 J** electrical input but gains only **30 J** translational kinetic energy. **Name two possible destinations of** the difference and **explain why the account needs** them.

Marzano check - circle: ① ② ③

02 Worked example: explain the prediction

Reference: $I = \Delta q/\Delta t$; $I = \mathbf{0}$ in an ideal open circuit.
Use the assigned simulation and teacher solder procedure. Disconnect power; hot irons/joints stay in the designated work area.

Worked reasoning: In a simple car circuit, battery positive connects through the switch and motor back to battery negative. A wire directly across the battery bypasses the motor and can create a hazardous short circuit.

Your turn: Draw the intended closed loop and circle a place where an open switch safely breaks it.



Marzano check - circle: ① ② ③

03 Read and explain the diagram or equation

1. **Draw your simulated closed circuit** and an open-switch version.
2. **Predict which runs the motor** and why.



Circuit symbols: long/short lines = battery; rectangles = resistors; M = motor.

Marzano check - circle: ① ② ③

04 Apply the physics

A test resistor has **6 V** across it and carries **0.30 A**.
1. **Calculate resistance** and power.
2. **Compare it** with the motor circuit shown: why might a running motor fail to behave like that fixed resistor?



Marzano check - circle: ① ② ③

Simulate a circuit and practice soldering

antocciphysics

Continue down each column.

05 Explain your reasoning

Make a two-column record: practice-joint observation and next improvement. Include teacher feedback on the joint and tool handling.

Observed joint / handling	Teacher feedback	Next time
___	___	___
___	___	___

Marzano check - circle: 1 2 3

06 Review: connect an earlier idea

Two equal **12 Ω** resistors are connected in parallel. **Find equivalent resistance**, then compare with a series connection of the same pair.
Draw the stated circuit and **label quantities relevant** to the question.

Draw the complete circuit and label shared nodes.

Marzano check - circle: 1 2 3

07 Exit check

Explain why a shiny joint alone does not show that the electrical and mechanical connection is reliable.



Marzano check - circle: 1 2 3

08 STRETCH: test the prediction

A **6 V** motor circuit is modeled with **3 ohms** while running and **1 ohm** at stall. **Compare currents** and input powers; **explain why resistance**/current may change with motion and what this calculation leaves out.



Marzano check - circle: 1 2 3