Ohm’s law

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Connect voltage, current and resistance for an ohmic component.

SUCCESS CRITERIA - I can...

1. Identify the voltage across a resistor.
2. Use V=IR with appropriate units.
3. Predict changes while stating what stays fixed.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

LANGUAGE GOAL Use “ohmic” and “resistance” to explain your model or result. Sentence starters are optional.

ohmic: having constant resistance under the stated physical conditions

resistance: voltage divided by current for a stated operating condition

voltage: electric potential difference; energy transferred per charge

01 Warm-up: bring back an earlier idea

An electric field of 5 N/C points left.
Draw the force direction on +3 C and on -3 C, then compare sizes.

Word help: electric field = force per positive test charge at a location

Sentence starter: Both … . They differ in … because … .

Marzano check - circle: ① ② ③

02 Worked example: explain the model

Reference: V = IR; I = V/R.
Ohmic resistor under fixed physical conditions. Resistance can change with temperature.

Worked reasoning: Across a 4 ohm resistor, a 12 V supply gives I=V/R=3 A. Doubling resistance at the same voltage halves current.

Your turn: Draw a one-resistor circuit, label supply voltage and current, and mark both resistor terminals.

Sentence starter: The … in my model represents … . Its label shows … .



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

Ohm’s law

antocciphysics


Continue down each column.

Sentence starters are optional. You may plan in any language.

03 Read and interpret the model

Sketch a graph of V against I for a fixed ohmic resistor. What does its slope represent?

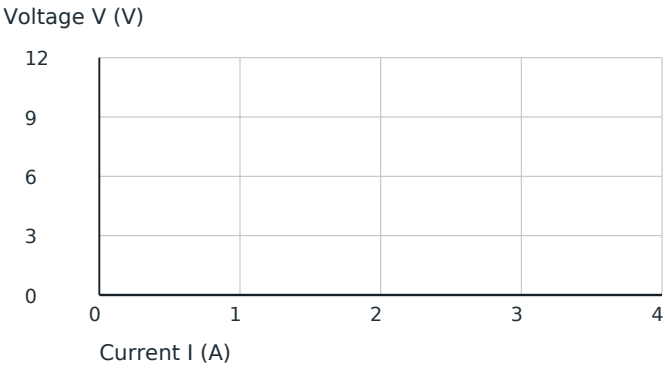Sentence starter: The … in my model represents … . Its label shows … .



Marzano check - circle: ① ② ③

04 Apply the physics

A 6 V lab supply is connected across a 3 Ω resistor.
Label the closed circuit and calculate current.
Show the conventional-current direction through the resistor.

Sentence starter: I found … [unit]. This value means … in this situation.



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

Ohm’s law

antocciphysics

Continue down each column.

Sentence starters are optional. You may plan in any language.

05 Explain your reasoning

A student doubles resistance while keeping voltage fixed and predicts twice the current. Correct the prediction.

Sentence starter: I predict … . My model supports this because … .

Marzano check - circle: 1 2 3

06 Review: connect an earlier idea

Two EM waves in vacuum have frequencies f and 4 f.
Compare speeds and wavelengths.
Label a wave sketch to support the calculation or comparison.

Word help: vacuum = space with negligible matter

Sentence starter: Both … . They differ in … because … .



Time or position: choose and label

Marzano check - circle: 1 2 3

07 Exit check

Find voltage across a 4 Ω resistor carrying 2 A.

Sentence starter: I found … [unit]. This value means … in this situation.



Label component values, current and voltage as needed.

Marzano check - circle: 1 2 3

08 STRETCH: test the model

Find three voltage-resistance pairs giving 2 A. Which comparison isolates the effect of resistance?

Sentence starter: I found … [unit]. This value means … in this situation.



Label component values, current and voltage as needed.

Marzano check - circle: 1 2 3