Current: charge flow rate

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Calculate current as charge transferred per time.

SUCCESS CRITERIA - I can...

1. Use I=q/t with seconds and coulombs.
2. Describe conventional current direction.
3. Explain steady charge conservation at a junction.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

01 Warm-up: bring back an earlier idea

Keep charge separation fixed and multiply one charge magnitude by 3. Compare electric-force magnitude.

Marzano check - circle: ① ② ③

02 Worked example: explain the model

Reference: I = Δq/Δt.
Current is charge per time; 1 A = 1 C/s. Conventional current follows positive charge motion.

Worked reasoning: If 12 C pass a point in 4 s, average current is I=Q/t=3 A. Charge circulates; a resistor does not consume charge.

Your turn: Draw a complete loop and label equal current before and after one resistor in steady state.



Label component values, current and voltage as needed.

Marzano check - circle: ① ② ③

03 Read and interpret the model

Draw conventional current around the closed circuit, outside the battery from + toward -. What happens if a wire is disconnected?




Circuit symbols: long/short lines = battery; rectangles = resistors.

Marzano check - circle: ① ② ③

04 Apply the physics

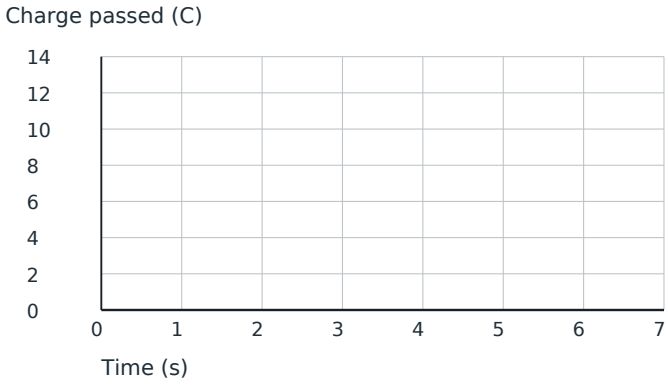During a circuit test, 12 C passes one point in a wire over 7 s. Plot cumulative charge against time for a constant current. Calculate current from the graph's slope.



Marzano check - circle: ① ② ③

Current: charge flow rate

antocciphysics

Continue down each column.

05 Explain your reasoning

At a junction, 5 A enters and 2 A leaves along one branch. Find the other outgoing current in steady operation. Explain the conservation rule.

Marzano check - circle: 1 2 3

06 Review: connect an earlier idea

A siren emits 600 Hz steadily while approaching a stationary listener. Compare observed and emitted frequency and explain.
Use wavefront spacing to explain the frequency change.

Source moves right. Add wavefronts.



Marzano check - circle: 1 2 3

07 Exit check

A current of 2 A flows for 3 s. How much charge passes?



Label component values, current and voltage as needed.

Marzano check - circle: 1 2 3

08 STRETCH: test the model

Construct two charge -time pairs that both give 2 A. Explain why different total charges can give the same current.



Label component values, current and voltage as needed.

Marzano check - circle: 1 2 3