Plan the electric car

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Use circuit and mechanical evidence to plan a controlled motor-car test.

SUCCESS CRITERIA - I can...

1. Draw the battery-switch-motor circuit.
2. Predict effects of an open switch and a changed connection.
3. Plan one controlled performance comparison.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

LANGUAGE GOAL Use “circuit” and “motor” to explain your model or result. Sentence starters are optional.

circuit: a connected arrangement of electrical components

motor: a device converting electrical energy to mechanical output

constraint: a requirement or limit that the design must meet

01 Bring back an earlier idea

A magnet moves through a 50-turn coil. Propose two controlled changes that could increase induced-emf magnitude and explain each.

Word help: emf = energy supplied per charge, measured in volts

Sentence starter: My claim is … . The diagram/data show …, so … .

Marzano check - circle: ① ② ③

02 Explain a worked example

Reference: $P = IV$; $E = P\Delta t$.

Constant power model. Use approved battery, switch and motor. Disconnect before rewiring; keep wheels clear for first power.

Worked reasoning: A classroom car circuit uses a battery, switch and motor in one closed loop. The switch opens the current path; a chassis drawing must also reserve space for safe wiring and moving parts.

Your turn: Draw the circuit separately from a labeled component-placement plan.

Sentence starter: My design shows … . It meets the requirement by … .

Marzano check - circle: ① ② ③

03 Look and explain

Draw and label the battery, switch, motor and wires as a complete loop.
Mark a location where an open connection stops current.

Sentence starter: The … in my model represents … . Its label shows … .



Circuit symbols: long/short lines = battery; rectangles = resistors; M = motor.

Marzano check - circle: ① ② ③

Plan the electric car

antocciphysics

Continue down each column.

Sentence starters are optional. You may plan in any language.

04 Build the solution

A supplied test car travels 4 m in 4 s.
Find average speed. Prepare columns for your team's actual distance and time measurements.

Sentence starter: I found ... [unit]. This value means ... in this situation.

Trial	Distance (m)	Time (s)
1		
2		
3		

Marzano check - circle: 1 2 3

05 Use the idea

Your team changes wheels, battery and axle alignment together and gets a faster run. Can you attribute the change to wheels alone?
Explain a better comparison.

Sentence starter: My claim is ... . The diagram/data show ..., so ... .

Marzano check - circle: 1 2 3

06 Choose a method

A current of 4 A flows for 6 s.
Find the charge that passes.

Word help: current = rate of charge flow

Sentence starter: I found ... [unit]. This value means ... in this situation.

Marzano check - circle: 1 2 3

07 Exit check

List one safety check and one measurement you need before the first powered test.

Sentence starter: I notice ... . This supports ... because ... .

Marzano check - circle: 1 2 3

08 STRETCH: Apply it another way

Design two switch placements that both interrupt the same series motor circuit.
Explain one practical reason to choose between them.

Sentence starter: My design shows ... . It meets the requirement by ... .

Marzano check - circle: 1 2 3