Circuit investigation

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Use measurements to test a circuit model safely.

SUCCESS CRITERIA - I can...

1. Draw and predict before powering a circuit.
2. Place ammeters in series and voltmeters in parallel.
3. Compare measured and predicted values using evidence.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

LANGUAGE GOAL Use “ammeter” and “voltmeter” to explain your model or result. Sentence starters are optional.

ammeter: an instrument placed in series to measure current

voltmeter: an instrument placed across two points to measure voltage

trial: one run or repetition of a test

01 Bring back an earlier idea

A circuit has 3 identical series resistors. Add two more at unchanged ideal supply voltage.
Compare new current with the original.

Word help: current = rate of charge flow

Sentence starter: Both ... . They differ in ... because ... .

Marzano check - circle: ① ② ③

02 Explain a worked example

Reference: V = IR.
Use approved low voltage. Ammeter in series; voltmeter across a component. Disconnect before rewiring; never put an ammeter across the supply.

Worked reasoning: Supplied measurements show V=2, 4, 6 V and I=0.2, 0.4, 0.6 A. Each V/I is 10 ohms. This supports an ohmic model over the measured range.

Your turn: Plot V against I and mark the slope.
State why the data do not prove the model at every possible temperature or voltage.

Sentence starter: Under the assumption ..., the evidence ... supports ... because ... .

Marzano check - circle: ① ② ③

03 Represent and interpret

On a resistor circuit sketch, add an ammeter to measure loop current and a voltmeter to measure the resistor’s drop.

Sentence starter: The ... in my model represents ... . Its label shows ... .



Circuit symbols: long/short lines = battery; rectangles = resistors.

Marzano check - circle: ① ② ③

04 Solve and justify

A supplied trial gives V=5.8 V and I=.46 A for a nominal 12 Ω resistor.
Find measured V/I and relative deviation from 12 Ω.
Name a plausible uncertainty source.

Sentence starter: I found ... [unit]. This value means ... in this situation.

Marzano check - circle: ① ② ③

Read down the left column, then down the right. Use the open space to draw, calculate and explain.

Circuit investigation

antocciphysics

Continue down each column.

Sentence starters are optional. You may plan in any language.

05 Analyze the reasoning

A reading disagrees with your prediction. List two checks before replacing the model or deleting data.

Sentence starter: I predict … . My model supports this because … .

Marzano check - circle: 1 2 3

06 Choose a method

An ideal blackbody has peak wavelength 580 nm.
Use $\lambda_{max}\,T = 2.90\times10^{6}$ nm·K.
Estimate temperature.

Word help: blackbody = an ideal absorber/emitter used in a thermal-radiation model

Sentence starter: I found … [unit]. This value means … in this situation.

Marzano check - circle: 1 2 3

07 Exit check

Design a three-point V-I test.
State what to control and what pattern would support constant resistance.

Sentence starter: My design shows … . It meets the requirement by … .

Marzano check - circle: 1 2 3

08 STRETCH: Apply it another way

Two readings are 3.0±0.1 V and 0.30±0.02 A.
Find central resistance and worst-case bounds.

Sentence starter: I found … [unit]. This value means … in this situation.

Marzano check - circle: 1 2 3