Plan the electric car

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Use circuit and mechanical evidence to plan a controlled motor-car test.

SUCCESS CRITERIA - I can...

1. Draw the battery-switch-motor circuit.
2. Predict effects of an open switch and a changed connection.
3. Plan one controlled performance comparison.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

LANGUAGE GOAL Use “circuit” and “motor” to explain your model or result. Sentence starters are optional.

circuit: a connected arrangement of electrical components

motor: a device converting electrical energy to mechanical output

constraint: a requirement or limit that the design must meet

01 Bring back an earlier idea

The same flux change through the same coil occurs in 1/3 of the time.
Compare induced-emf magnitude and name a condition for that comparison.

Word help: flux = a measure of magnetic field passing through a chosen area

Sentence starter: Both … . They differ in … because … .

Marzano check - circle: ① ② ③

02 Explain a worked example

Reference: $P = IV$; $E = P\Delta t$.
Constant power model. Use approved battery, switch and motor. Disconnect before rewiring; keep wheels clear for first power.

Worked reasoning: A classroom car circuit uses a battery, switch and motor in one closed loop. The switch opens the current path; a chassis drawing must also reserve space for safe wiring and moving parts.

Your turn: Draw the circuit separately from a labeled component-placement plan.

Sentence starter: My design shows … . It meets the requirement by … .

Marzano check - circle: ① ② ③

03 Represent and interpret

Draw and label the battery, switch, motor and wires as a complete loop.
Mark a location where an open connection stops current.

Sentence starter: The … in my model represents … . Its label shows … .



Circuit symbols: long/short lines = battery; rectangles = resistors; M = motor.

Marzano check - circle: ① ② ③

04 Solve and justify

A supplied motor draws .50 A at 3 V for a 6 s run. The car travels 5 m.
Find input power, input energy and average speed.

Sentence starter: I found … [unit]. This value means … in this situation.

Marzano check - circle: ① ② ③

Plan the electric car

antocciphysics

Continue down each column.

Sentence starters are optional. You may plan in any language.

05 Analyze the reasoning

Your team changes wheels, battery and axle alignment together and gets a faster run. Can you attribute the change to wheels alone?
Explain a better comparison.

Sentence starter: Under the assumption …, the evidence … supports … because … .

Marzano check - circle: 1 2 3

06 Choose a method

Electrons in a wire drift at 0.4 mm/s while a lamp responds quickly after a switch closes.
Explain why response time cannot be found by timing one electron across the wire.

Sentence starter: Under the assumption …, the evidence … supports … because … .

Marzano check - circle: 1 2 3

07 Exit check

Name two reasons electrical input energy will exceed the car’s final translational kinetic energy.

Sentence starter: I notice … . This supports … because … .

Marzano check - circle: 1 2 3

08 STRETCH: Apply it another way

A 6 V motor draws 0.8 A normally and 2.4 A when stalled in supplied test data.
Compare input powers and explain a test plan that avoids prolonged stall.

Sentence starter: Both … . They differ in … because … .

Marzano check - circle: 1 2 3