Combination circuits

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Reduce a circuit by identifying genuine series and parallel groups.

SUCCESS CRITERIA - I can...

1. Identify nodes before grouping resistors.
2. Reduce one group at a time.
3. Check current and voltage conservation in the original circuit.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

01 Bring back an earlier idea

Measured (I, V) pairs are (0.10, 3), (0.20, 6), (0.30, 9) in A, V. Find resistance and explain the evidence for an ohmic model.

Marzano check - circle: ① ② ③

02 Explain a worked example

Reference: $R_{series} = R_1 + R_2$; $1/R_{parallel} = 1/R_1 + 1/R_2$; $V = IR$. Reduce one known group at a time. Check nodes before calling components series or parallel.

Worked reasoning: A 2 ohm resistor is in series with two 4 ohm resistors in parallel. The parallel pair equals 2 ohms; total 4 ohms. A 12 V supply gives 3 A total.

Your turn: Draw the network and label the two series sections before splitting the branch current.

Marzano check - circle: ① ② ③

03 Represent and interpret

A 2 Ω resistor is in series with two parallel 6 Ω resistors. Draw the arrangement and circle the parallel group.



Circuit symbols: long/short lines = battery; rectangles = resistors.

Marzano check - circle: ① ② ③

04 Solve and justify

For that circuit with a 10 V battery, calculate the parallel equivalent. Find the series drop, branch voltage and each branch current.

Marzano check - circle: ① ② ③

Combination circuits

antocciphysics

Continue down each column.

05 Analyze the reasoning

A student adds all three resistor values because they are drawn side by side. What should determine the grouping instead?

Marzano check - circle: 1 2 3

06 Choose a method

Two targets each have range 600 m but different radial velocities. Explain how they can have equal echo delays yet different Doppler shifts.

Marzano check - circle: 1 2 3

07 Exit check

Replace the two 6 Ω branches with 3 Ω and 6 Ω. Keep the 2 Ω series resistor and 10 V supply. Find total current.

Marzano check - circle: 1 2 3

08 STRETCH: Apply it another way

A 3 ohm series resistor feeds parallel 6 and 3 ohm branches from 15 V. Find total current, voltage across parallel section and each branch current.

Marzano check - circle: 1 2 3