Plan the electric car

antocciphysics

Name: _____ **Block:** _____ (teacher only) **Mastery Rating:** _____

LEARNING TARGET Use circuit and mechanical evidence to plan a controlled motor-car test.

SUCCESS CRITERIA - I can...

1. Draw the battery-switch-motor circuit.
2. Predict effects of an open switch and a changed connection.
3. Plan one controlled performance comparison.

Core: teacher selects from 1-7. **Stretch:** 8 after checking your work.

MARZANO SELF-CHECK

① Need help starting

② Can do part; need help

③ Solve and explain with allowed supports

01 Bring back an earlier idea

The same flux change through the same coil occurs in 1/3 of the time. Compare induced-emf magnitude and name a condition for that comparison.

Marzano check - circle: ① ② ③

02 Explain a worked example

Reference: P = IV; E = PΔt.
Constant power model. Use approved battery, switch and motor. Disconnect before rewiring; keep wheels clear for first power.

Worked reasoning: A classroom car circuit uses a battery, switch and motor in one closed loop. The switch opens the current path; a chassis drawing must also reserve space for safe wiring and moving parts.

Your turn: Draw the circuit separately from a labeled component-placement plan.

Marzano check - circle: ① ② ③

03 Represent and interpret

Draw and label the battery, switch, motor and wires as a complete loop. Mark a location where an open connection stops current.



Circuit symbols: long/short lines = battery; rectangles = resistors; M = motor.

Marzano check - circle: ① ② ③

04 Solve and justify

A supplied motor draws .50 A at 3 V for a 6 s run. The car travels 5 m. Find input power, input energy and average speed.

Marzano check - circle: ① ② ③

Plan the electric car

antocciphysics

Continue down each column.

05 Analyze the reasoning

Your team changes wheels, battery and axle alignment together and gets a faster run. Can you attribute the change to wheels alone? Explain a better comparison.

Marzano check - circle: 1 2 3

06 Choose a method

Electrons in a wire drift at 0.4 mm/s while a lamp responds quickly after a switch closes. Explain why response time cannot be found by timing one electron across the wire.

Marzano check - circle: 1 2 3

07 Exit check

Name two reasons electrical input energy will exceed the car’s final translational kinetic energy.

Marzano check - circle: 1 2 3

08 STRETCH: Apply it another way

A 6 V motor draws 0.8 A normally and 2.4 A when stalled in supplied test data. Compare input powers and explain a test plan that avoids prolonged stall.

Marzano check - circle: 1 2 3